## Series Circuit Assembly

- •Try this circuit with one Cr2032 battery positive side UP first.
- Record results.
- •Make a Maker Tape™ tape loop and place it on the battery already in place.
- •Stick a second Cr2032 battery on top of the first battery by tape loop so the positive side is also up.
- Retest.
- Record results.

